

Digital Design with the Verilog HDL

Chapter 3: Hierarchy & Simulation

Binh Tran-Thanh

Department of Computer Engineering
Faculty of Computer Science and Engineering
Ho Chi Minh City University of Technology

May 26, 2023



Module Port List Declaration (Multiple ways)

```
module Add_half(c_out, sum, a, b);
    output sum, c_out;
    input a, b;
    ...
endmodule
//*****
module Add_half(output c_out, sum, input a, b);
    ...
endmodule
//*****
module xor_8bit(out, a, b);
    output[7:0] out;
    input[7:0] a, b;
    ...
endmodule
//*****
module xor_8bit(output[7:0] out, input[7:0] a, b);
    ...
endmodule
```

Structural Design Tip

- If a design is complex, draw a block diagram!
- Label the signals connecting the blocks
- Label ports on blocks if not primitives/obvious.
- Easier to double-check your code!
- Don't bother with *300-gate design* ...
- But if that **big**, probably should use hierarchy!



Example: Hierarchy Multiplexer

```
module mux_8to1(output out,
                  input in0, in1, in2, in3, in4, in5, in6, in7,
                  input[2:0] select );


    ...
endmodule

//*****[mux2to1 as submodule]*****
module mux_2to1( output out, input in0, in1, select);
    wire n0, n1, n2;

    ...
endmodule
```



8to1 Mux from 2to1 Muxs Structure

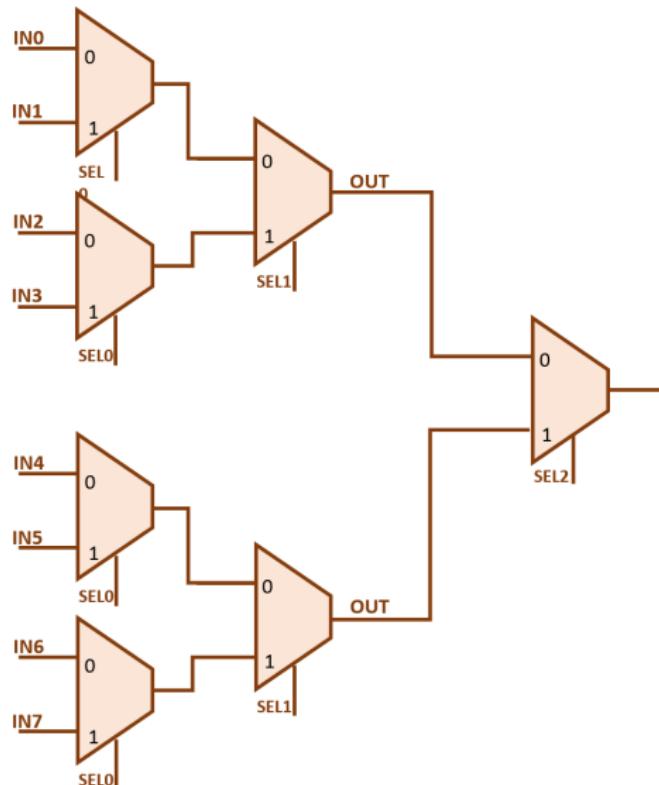

source: <https://vlsiuniverse.blogspot.com>

Interface: Hierarchical Multiplexer

```
module mux_8to1(output out,
                  input in0, in1, in2, in3, in4, in5, in6, in7,
                  input[2:0] select);
  wire n0, n1, n2, n3, n4, n5;

  //**** [level 1: 4 MUX2to1] ****/
  mux_2to1 M1_L1 (n0, in0, in1, select[0]),
             M2_L1 (n1, in2, in3, select[0]),
             M3_L1 (n2, in4, in5, select[0]),
             M4_L2 (n3, in6, in7, select[0]);
  //**** [level 2: 2 MUX2to1] ****/
  mux_2to1 M1_L2 (n4, n0, n1, select[1]),
             M2_L2 (n5, n2, n3, select[1]);
  //**** [level 3: 1 MUX2to1] ****/
  mux_2to1 M1_L3 (out, n4, n5, select[2]);
endmodule
```

Timing Controls For Simulation

- Can put “delays” in a Verilog design
 - Gates, wires, even behavioral statements!
- SIMULATION
 - Used to approximate “real” operation while simulating.
 - Used to control testbench
- SYNTHESIS
 - Synthesis tool IGNORES these timing controls
 - Cannot tell a gate to wait 1.5 nanoseconds!
 - Delay is a result of physical properties!
 - Only timing (easily) controlled is on **clock-cycle** basis
 - Can tell synthesizer to attempt to meet cycle-time restriction



Zero Delay vs. Unit Delay


- When no timing controls specified: zero delay
 - Unrealistic –even electrons take time to move
 - OUT is updated same time A and/or B change:
and (**OUT**, **A**, **B**)
- Unit delay often used
 - Not accurate either, but closer...
 - “Depth” of circuit does affect speed!
 - Easier to see how changes propagate through circuit
 - OUT is updated 1 “unit” after A and/or B change:
and #1 AO(OUT, A, B);



Zero/Unit Delay Example

Zero Delay					
T	A	B	C	Y	Z
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	1	1
4	1	0	0	0	1
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1
8	0	0	0	0	0
9	0	0	1	0	0
10	0	1	0	0	0
11	0	1	1	1	1
12	1	0	0	0	1
13	1	0	1	0	1
14	1	1	0	0	1
15	1	1	1	0	1

Unit Delay					
T	A	B	C	Y	Z
0	0	1	0	x	x
1	0	1	0	0	x
2	0	1	0	0	0
3	0	1	1	0	0
4	0	1	1	1	0
5	0	1	1	1	1
6	1	0	0	1	1
7	1	0	0	0	1
8	1	1	1	0	1
9	1	1	1	1	1
10	1	0	0	1	1
11	1	0	0	0	1
12	0	1	0	0	1
13	0	1	0	0	0
14	0	1	1	0	0
15	0	1	1	1	0
16	0	1	1	1	1

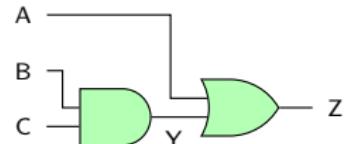

Zero Delay: Y and Z change at same “time” as A, B, and C!

Unit Delay: Y changes 1 unit after B, C

Unit Delay: Z changes 1 unit after A, Y



Types Of Delays

- Inertial Delay (Gates)
 - Suppresses pulses shorter than delay amount
 - In reality, gates need to have inputs held a certain time before output is accurate
 - This models that behavior
- Transport Delay (Nets)
 - “Time of flight” from source to sink
 - Short pulses transmitted
- Not critical for most of class
 - May need to know when debugging
 - Good to know for building very accurate simulation



Delay Examples

```
wire #5 net_1;           // 5 units transport delay  
  
and #4 (z_out, x_in, y_in); // 4 units inertial delay  
  
assign #3 z_out= a & b;    // 3 units inertial delay  
  
wire #2 z_out;           // 2 units transport delay  
and #3 (z_out, x_in, y_in); // 3 for gate, 2 for wire  
  
wire #3 c;               // 3 units transport delay  
assign #5 c = a & b;      // 5 for assign, 3 for wire
```





Delays In Testbenches

- Most common use in class
- Single testbench tests many possibilities
 - Need to examine each case separately
 - Spread them out over “time”
- Use to generate a clock signal
 - Example later in lecture



Simulation

Update only if changed

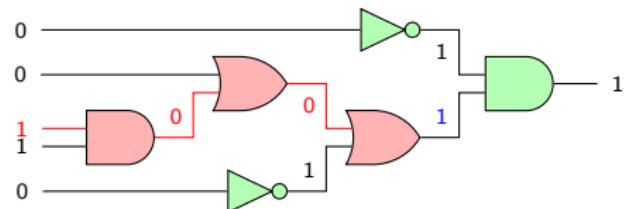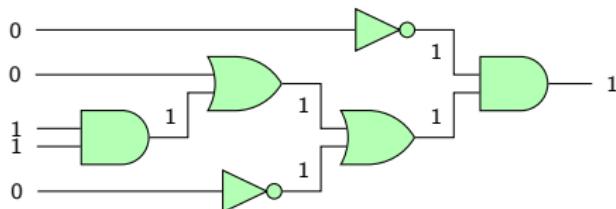


Some circuits are very large

- Updating every signal \Rightarrow very slow simulation
- Event-driven simulation is much faster!



Simulation of Verilog

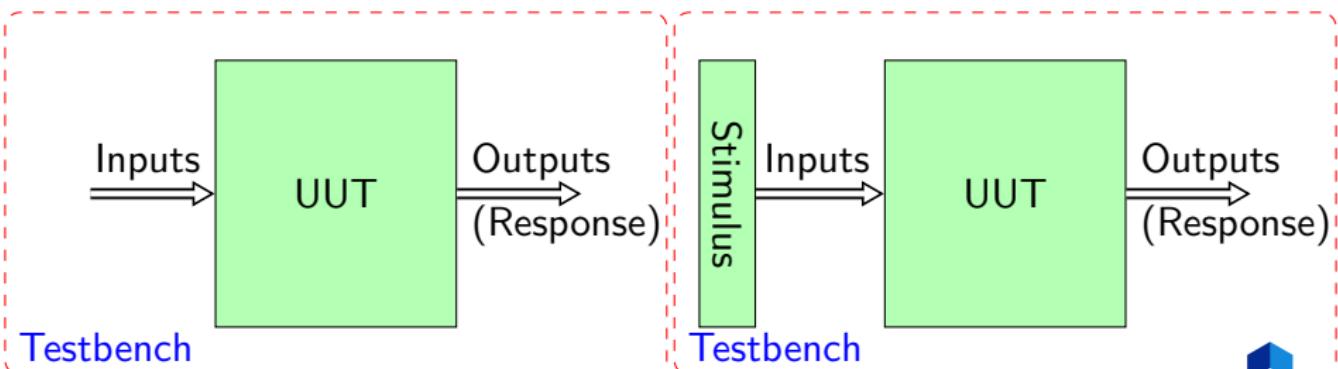- Need to verify your design
 - “Unit Under Test” (UUT)
- Use a “testbench”!
 - Special Verilog module with no ports
 - Generates or routes inputs to the UUT
 - Outputs information about the results




Simulation [Functionality] Example

```
module adder4b (sum, c_out, a, b, c_in);
    input [3:0] a, b;
    input c_in;
    output [3:0] sum;
    output c_out;

    assign {c_out, sum} = a + b + c_in;

endmodule
```

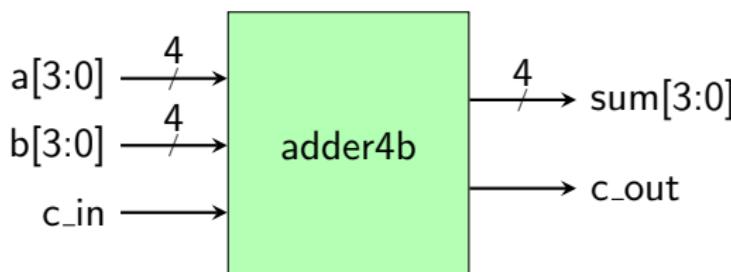


Simulation [Timing and Functionality] Example


```
'timescale 1ns /1ns          // time_unit/time_precision
module adder4b_delay (sum, c_out, a, b, c_in);
    input [3:0] a, b;
    input c_in;
    output [3:0] sum;
    output c_out;

    assign #5 {c_out, sum} = a + b + c_in;

endmodule
```

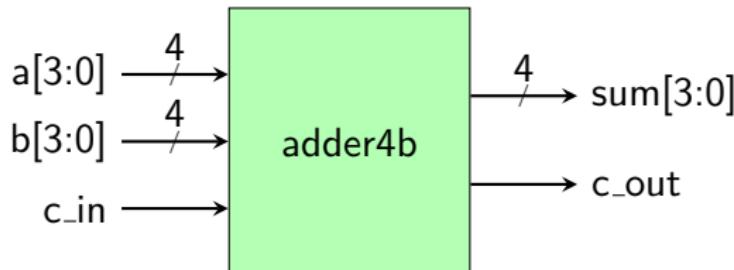

Simulation Example

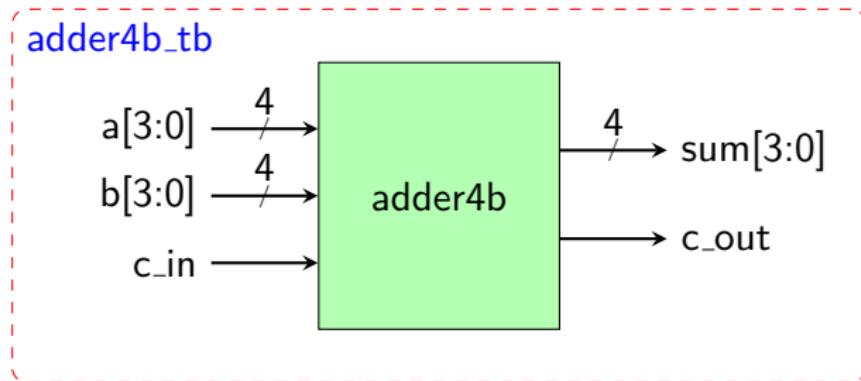


Testbenches frequently named (should NOT mix style)

- <UUT name>_tb.v (recommend)
- <UUT name>_t.v
- tb_<UUT name>.v
- t_<UUT name>.v

Testbench Example

```
'timescale 1ns /1ns          // time_unit/time_precision
module adder4b_tb;
    reg [3:0] in_a, in_b;    // inputs to UUT are regs
    reg c_in;                // inputs to UUT are regs
    wire [3:0] sum, sum_d;   // outputs of UUT are wires
    wire c_out, c_cout_d;    // outputs of UUT are wires
    // instantiate UUT
    adder4b      A1 (sum, c_out, in_a, in_b, c_in);
    adder4b_delay A2 (sum_d, c_cout_d, in_a, in_b, c_in);
    // stimulus generation
    initial begin
        {in_a, in_b, c_in} = 9'b0000_0000_0; // at 0 ns
        #10 {in_a, in_b, c_in} = 9'b1100_0100_1; // at 10 ns
        #10 {in_a, in_b, c_in} = 9'b0011_0110_1; // at 20 ns
        #10 {in_a, in_b, c_in} = 9'b1111_0001_0; // at 30 ns
        #10 {in_a, in_b, c_in} = 9'b0001_1111_0; // at 40 ns
        #10 $stop; // at 50 ns, stops simulation
    end
endmodule
```

Testbench Waveform

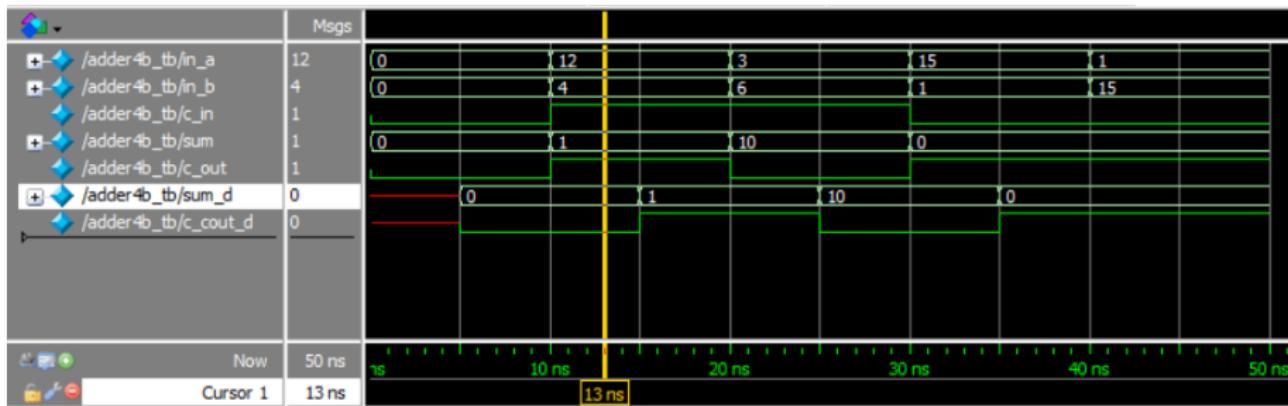

Testbench Requirements

- Instantiate the unit being tested (UUT)
- Provide input to that unit
 - Usually a number of different input combinations!
- Watch the “results” (outputs of UUT)
 - Can watch ModelSimWave window...
 - Can print out information to the screen or to a file



Output Test Info

- Several different system calls to output info
 - **\$monitor**
 - Output the given values whenever one changes
 - Can use when simulating Structural, RTL, and/or Behavioral
 - **\$display, \$strobe**
 - Output specific information as if printf or cout in a program
 - Used in Behavioral Verilog
- Can use formatting strings with these commands
- Only means anything in simulation
- Ignored by synthesizer



Output Format Strings

- Formatting string

`%h, %H hex`

`%d, %D decimal`

`%o, %O octal`

`%b, %B binary`

`%t time`

- `$monitor("%t: %b %h %h %b\n", $time, c_out, sum, a, b, c_in);`
- Can get more details from Verilog standard



Output Example

```
'timescale 1ns /1ns      // time_unit/time_precision
module adder4b_tb;
    reg [3:0] in_a, in_b; // inputs to UUT are regs
    reg c_in;           // inputs to UUT are regs
    wire [3:0] sum;     // outputs of UUT are wires
    wire c_out;         // outputs of UUT are wires
    // instantiate UUT
    adder4b UUT(sum, c_out, in_a, in_b, c_in);
    // monitor statement
    initial $monitor("time %t: cout=%b,sum=%h, in_a=%h, in_b
    =%h, cin=%b\n", $time, c_out, sum, in_a, in_b, c_in);
    // stimulus generation
    initial begin
        {in_a, in_b, c_in} = 9'b0000_0000_0; // at 0 ns
        #10 {in_a, in_b, c_in} = 9'b1100_0100_1; // at 10 ns
        #10 {in_a, in_b, c_in} = 9'b0011_0110_1; // at 20 ns
        #10 {in_a, in_b, c_in} = 9'b1111_0001_0; // at 30 ns
        #10 {in_a, in_b, c_in} = 9'b0001_1111_0; // at 40 ns
        #10 $stop; // at 50 ns, stops simulation
    end
endmodule
```

Output Example Output [Text View]

Executed at

https://www.tutorialspoint.com/compile_verilog_online.php

```
time 0: cout=0, sum=0, in_a=0, in_b=0, cin=0
time 10: cout=1, sum=1, in_a=c, in_b=4, cin=1
time 20: cout=0, sum=a, in_a=3, in_b=6, cin=1
time 30: cout=1, sum=0, in_a=f, in_b=1, cin=0
time 40: cout=1, sum=0, in_a=1, in_b=f, cin=0
```



Testbench (Read data input from file) Example

```
'timescale 1ns /1ns      // time_unit/time_precision
module adder4b_read_file_tb();
reg [3:0] in_a, in_b; // inputs to UUT are regs
reg c_in;           // inputs to UUT are regs
wire [3:0] sum;     // outputs of UUT are wires
wire c_out;         // outputs of UUT are wires
integer fd;          // file descriptors
// instantiate UUT
adder4b A1 (sum, c_out, in_a, in_b, c_in);
// monitor statement
initial $monitor("time %t: cout=%b,sum=%d, in_a=%d, in_b=%
    d, cin=%b", $time, c_out, sum, in_a, in_b, c_in);
// stimulus generation
initial begin
  fd = $fopen ("data.in", "r");
  if (fd) begin
    while ($fscanf (fd, "%h %h %b", in_a, in_b, c_in) != -1)
      begin
        #5;
      end
    end
    $fclose(fd); // close file handler
    $stop;       // finish simulation
  end // end initial
endmodule
```

DataIn file Example

data.in file

1 5 1

2 6 1

3 7 1

4 8 1

5 9 1

6 10 0

7 11 0

8 12 0

9 13 0

10 14 1

11 15 1



Testbench (Read input file, write output file) Example

```
'timescale 1ns /1ns      // time_unit/time_precision
module adder4b_read_file_write_output_tb();
reg [3:0] in_a, in_b; // inputs to UUT are regs
reg c_in;           // inputs to UUT are regs
wire [3:0] sum;     // outputs of UUT are wires
wire c_out;         // outputs of UUT are wires
integer read_fd, write_fd; // file descriptors
// instantiate UUT
adder4b A1 (sum, c_out, in_a, in_b, c_in);
// monitor statement
initial $monitor("time %t: cout=%b, sum=%d, in_a=%d, in_b
 =%d, cin=%b", $time, c_out, sum, in_a, in_b, c_in);
initial #100 $stop;
// stimulus generation
initial begin
read_fd = $fopen ("data.in", "r");
write_fd = $fopen ("data.out", "w");
if (write_fd ==0 && read_fd ==0) begin
$display("File was NOT opened successfully");
$stop; // stop
end

while ($fscanf (read_fd, "%d %d %b", in_a, in_b, c_in) !=
 -1) begin
$fdisplay (write_fd, "time %t: cout=%b, sum=%d, in_a=%d
 , in_b=%d, cin=%b", $time, c_out, sum, in_a, in_b, c_in)
;
#5;
end

$fclose(read_fd); // close read file handler
$fclose(write_fd); // close write file handler

end // end initial
endmodule
```

Exhaustive Testing

- For combinational designs w/ up to 8 or 9 inputs
 - Test ALL combinations of inputs to verify output
 - Could enumerate all test vectors, but don't ...
 - Generate them using a “for” loop!

```
reg[4:0] x;  
initial begin  
    // Remember to check infinite loop  
    // This example uses 5-bit counter for 16 samples  
    for(x = 0; x < 16; x = x + 1)  
        #5 ;           // need a delay here!  
    end
```

- Need to use “reg” type for loop variable?

Example: UUT

```
module Comparator4b(A_gt_B, A_lt_B, A_eq_B, A, B);
    output A_gt_B, A_lt_B, A_eq_B;
    input [3:0] A, B;

    // RTL Styles
    assign A_eq_B = (A == B)? 1 : 0;
    assign A_gt_B = (A > B) ? 1 : 0;
    assign A_lt_B = (A < B) ? 1 : 0;

endmodule
```



Example: Testbench

```
module Comparator4b_tb;
    wire A_gt_B, A_lt_B, A_eq_B;
    reg [4:0] A, B; // 5-bit to prevent loop wrap around
    // UUT
    Comparator4b M1(A_gt_B, A_lt_B, A_eq_B, A[3:0], B[3:0]);
    initial $monitor("%t: A=%h, B=%h, AgtB=%b, AltB=%b, AeqB
    =%b", $time, A[3:0], B[3:0], A_gt_B, A_lt_B, A_eq_B);
    initial #2000 $finish; // end simulation, quit program
    initial begin
        #5;
        /** After #5, exhaustive test of valid inputs ***/
        for (A = 0; A < 16; A = A + 1) begin
            for (B = 0; B < 16; B = B + 1) begin
                #5; // every 5 time unit, A, B will be updated
            end // first for
        end // second for
    end // initial
endmodule
```

Example: Testbench Output [Text view]

Executed at

https://www.tutorialspoint.com/compile_verilog_online.php

```
0: A=x, B=x, AgtB=x, AltB=x, AeqB=x
5: A=0, B=0, AgtB=0, AltB=0, AeqB=1
10: A=0, B=1, AgtB=0, AltB=1, AeqB=0
15: A=0, B=2, AgtB=0, AltB=1, AeqB=0
.....
75: A=0, B=e, AgtB=0, AltB=1, AeqB=0
80: A=0, B=f, AgtB=0, AltB=1, AeqB=0
85: A=1, B=0, AgtB=1, AltB=0, AeqB=0
90: A=1, B=1, AgtB=0, AltB=0, AeqB=1
95: A=1, B=2, AgtB=0, AltB=1, AeqB=0
.....
1275: A=f, B=e, AgtB=1, AltB=0, AeqB=0
1280: A=f, B=f, AgtB=0, AltB=0, AeqB=1
1285: A=0, B=0, AgtB=0, AltB=0, AeqB=1
```

Combinational Testbench

```
module comb(output d, e, input a, b, c);
    and(d, a, b);
    nor(e, a, b, c);
endmodule

module comb_tb;
    wire d, e;
    reg [3:0] abc;
    comb CMD(d, e, abc[2], abc[1], abc[0]); // UUT
    initial $monitor("%t: a=%b, b=%b, c=%b, d=%b, e=%b",
                     $time, abc[2], abc[1], abc[0], d, e);
    initial #2000 $finish; // end simulation, quit program
    // exhaustive test of valid inputs
    initial begin
        for(abc= 0; abc< 8; abc= abc+ 1) begin #5; end // for
    end // initial
endmodule
```

Generating Clocks

- Wrong way:

```
initial begin
    #5 clk = 0;
    #5 clk = 1;
    #5 clk = 0;
    ...
    //((repeat hundreds of times))
end
```

- Right way:

```
initial
    clk = 0;
    always @ (clk)
        #5 clk = ~clk;
```

```
initial begin
    clk = 0;
    forever #5 clk = ~clk;
end
```

- LESS TYPING
- Easier to read, harder to make mistake

FSM Testing

- Response to input vector depends on state
- For each state:
 - Check all transitions
 - For Moore, check output at each state
 - For Mealy, check output for each transition
 - This includes any transitions back to same state!
- Can be time consuming to traverse FSM repeatedly...



Example : 3-bit Counter

- Write a testbench to test the 3-bit counter.

```
module Counter3b(output reg [2:0] counter_out, input  
clk, rst);  
  
// Structural style  
always @ (posedge clk) begin  
    if (rst) begin counter_out <= 3'b000; end  
    else begin counter_out <= counter_out + 1'b1; end  
end  
  
endmodule
```

- Initially reset the counter and then test all states, but do not test reset in each state.



3-bit Counter Testbench

```
module Counter3b_tb;
    wire [2:0] out;
    reg clk, rst;

    Counter3b counter(out, clk, rst); // UUT

    initial $monitor("%t: out=%b, rst=%b, clk=%b", $time, out
        , rst, clk);
    initial #100 $finish; // end simulation, quit program
    initial begin
        clk= 0;
        forever #5 clk= ~clk; // What is the clock period?
    end
    initial begin
        rst= 1;
        #10 rst= 0;
    end // end initial
endmodule
```

3-bit Counter Testbench Output [Text View]

```
Time 0: out=xxx, rst=1, clk=0
Time 5: out=000, rst=1, clk=1
Time 10: out=000, rst=0, clk=0
Time 15: out=001, rst=0, clk=1
Time 20: out=001, rst=0, clk=0
Time 25: out=010, rst=0, clk=1
Time 30: out=010, rst=0, clk=0
Time 35: out=011, rst=0, clk=1
Time 40: out=011, rst=0, clk=0
Time 45: out=100, rst=0, clk=1
Time 50: out=100, rst=0, clk=0
Time 55: out=101, rst=0, clk=1
Time 60: out=101, rst=0, clk=0
Time 65: out=110, rst=0, clk=1
Time 70: out=110, rst=0, clk=0
Time 75: out=111, rst=0, clk=1
Time 80: out=111, rst=0, clk=0
Time 85: out=000, rst=0, clk=1
Time 90: out=000, rst=0, clk=0
Time 95: out=001, rst=0, clk=1
Time 100: out=001, rst=0, clk=0
```


Force/Release In Testbenches

- Allows you to "override" value FOR SIMULATION
- Doesn't do anything in "real life"
 - No fair saying "if $2+2 == 5$, then force to 4" Synthesizer won't allow force...release anyway
- How does this help testing?
 - Can help to pinpoint bug
 - Can use with FSMs to override state
- Force to a state
 - Test all edges/outputs for that state
- Force the next state to be tested, and repeat
 - Can also use simulator force functionality



Force/Release Example

```
assign y = a & b;  
assign z = y | c;  
initial begin  
    a = 0; b = 0; c = 0;  
    #5 a = 0; b = 1; c = 0;  
    #5 force y = 1;  
    #5 b = 0;  
    #5 release y;  
    #5 $stop;  
end
```

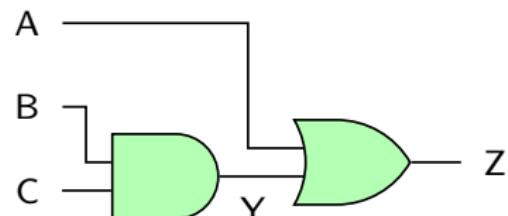

Time	a	b	c	y	z
0	0	0	0	0	0
5	0	1	0	0	0
10	0	1	0	1	1
15	0	0	0	1	1
20	0	0	0	0	0

